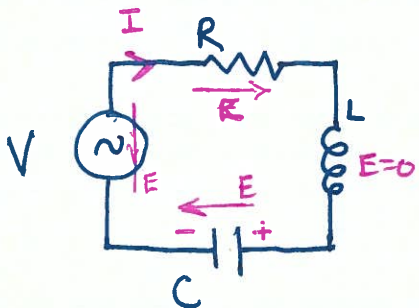


Driven RLC circuits, metal detectors



$$V = V_0 \cos(\omega t)$$

Recall, KVL does not really hold...
[that is, $\oint \mathbf{E} \cdot d\mathbf{l} \neq 0$]

$$IR + 0 + V_C - V_0 \cos \omega t = -L \frac{dI}{dt}$$

We know $I = \frac{dq}{dt}$...
and $V_C = Q/C$

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = V_0 \cos(\omega t)$$

Solution to RLC Circuit

Solution for Current in RLC (steady state)

$$I = \frac{V_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \cos(\omega t - \phi), \quad \tan \phi = \frac{\omega L - \frac{1}{\omega C}}{R}$$

$$\text{REACTANCE } X = \omega L - \frac{1}{\omega C}$$


$$\text{IMPEDANCE } Z = \sqrt{R^2 + X^2}$$

$\phi > 0$ means current lags voltage (inductor)

$\phi < 0$ means current leads voltage (capacitor)

$$\text{Current is } I = I_{\max} \cdot \cos(\omega t - \phi)$$

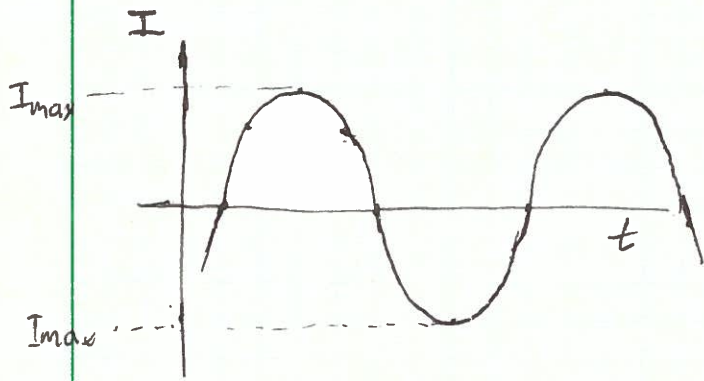
Resonance occurs when I_{\max} is greatest, when $\omega L = \frac{1}{\omega C}$



Fix RLC but change driving frequency ω ...

[1] $\omega \approx 0$ [DC], $Z \rightarrow \infty$, $I_{max} \rightarrow 0$
 (capacitor charges and acts as an open circuit, does not pass I)

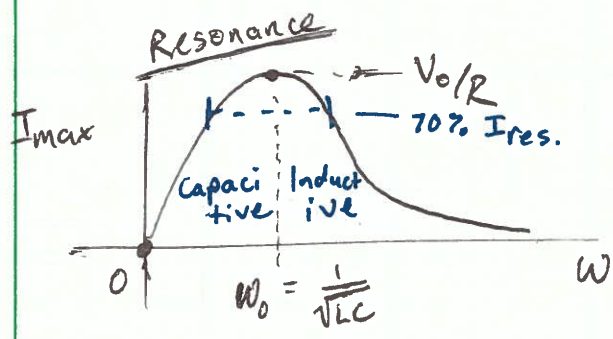[2] $\omega \rightarrow \infty$, $Z \rightarrow \infty$, $I_{max} \rightarrow 0$
 (due to inductor, self inductance dominates)



$$\Delta \omega = R/L$$

$$Q = \frac{\omega_0}{\Delta \omega} = \frac{1}{\sqrt{LC}} \cdot \frac{L}{R}$$

$$Q = \frac{1}{R} \sqrt{L/C} \quad \text{Quality factor}$$

$\Delta \omega$ at 70% of I_{max} is width at half power

DEMO : 200 W lightbulb in RLC circuits

$f = 60 \text{ Hz}$ ($\omega = 377 \text{ Hz}$)

$v = 110\sqrt{2} \cos(\omega t)$

$R = 60 \Omega$ hot 200W

$L = 0.1 \text{ H}$, $C = 8 \mu\text{F}$

So... $Z = 300 \Omega$
 $\omega L = 38 \Omega$, $\frac{1}{\omega C} = 332 \Omega$

and $\omega_0 = \frac{1}{\sqrt{LC}} = 1120 \text{ Hz}$

(note, $\omega = 377 \text{ Hz} \ll \omega_0 = 1120 \text{ Hz}$)
 so capacitance dominates!


$$I_{max} = \frac{V_0}{Z} = \frac{110\sqrt{2}}{300} \approx \frac{1}{2} \text{ A}$$

Power in bulb $= \frac{1}{2} I_{max}^2 R = \frac{1}{2} (0.5)^2 (60) = 7.5 \text{ W}$ too low power to turn on! 2/3
 (way below resonance)


Can we design the system better to light up the bulb? YES; change L, C to shift resonance!

If we shift resonance frequency down to $\omega_0 = 377$ Hz then resonance frequency equals driving frequency ($\omega = \omega_0$) and we are in resonance! (I_{max} is greatest)

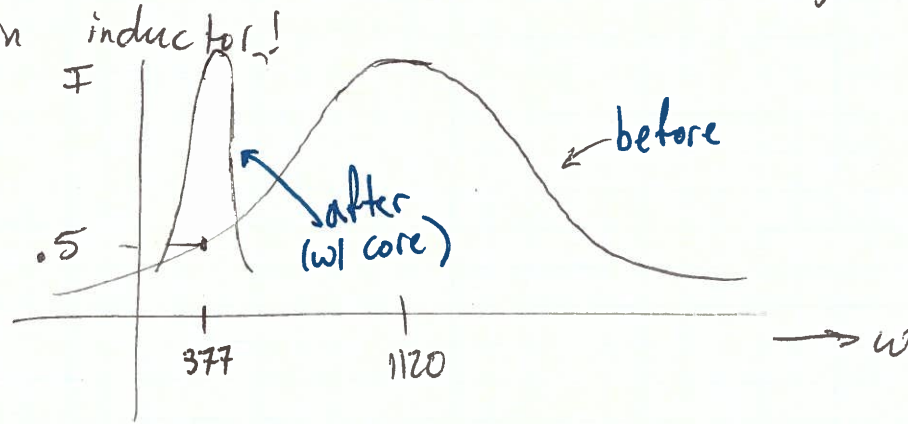Lewin chooses to increase L by inserting iron core in inductor!




Metal Detector

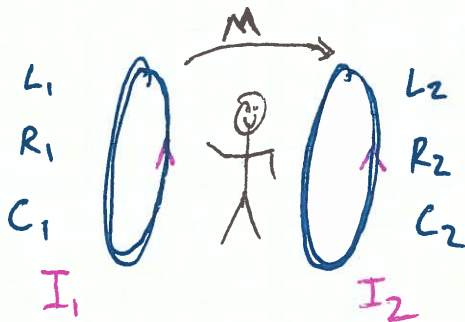

Mutual Inductance, M

Resonance

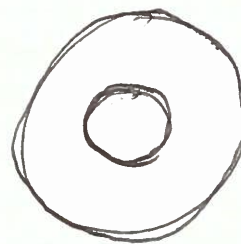

Ground Search Coil